

# The Processor: Single Cycle RISC-V and Pipelined RISC-V Basics

*[Adapted from Computer Organization and Design,  
Patterson & Hennessy, courtesy for Mary Jane Irwin]*


# The Processor: Datapath & Control

## ❑ Our implementation of the RISC-V is simplified

- ❑ memory-reference instructions: **ld, sd**
- ❑ arithmetic-logical instructions: **add, sub, and, or**
- ❑ control flow instructions: **beq**
 
## ❑ Generic implementation

- ❑ use the program counter (PC) to supply the instruction address and fetch the instruction from memory (and update the PC)
- ❑ decode the instruction (and read registers)
- ❑ execute the instruction




## ❑ All instructions use the ALU after reading the registers

How? memory-reference? arithmetic? control flow?
 
## Aside: Clocking Methodologies

- ❑ The **clocking methodology** defines when data in a state element is valid and stable relative to the clock
  - ❑ State elements - a memory element such as a register
  - ❑ Edge-triggered – all state changes occur on a clock edge
- ❑ Typical execution
  - ❑ read contents of state elements -> send values through combinational logic -> write results to one or more state elements




- ❑ Assumes state elements are written on every clock cycle; if not, need explicit write control signal
  - ❑ write occurs only when **both** the write control is asserted and the clock edge occurs

# Fetching Instructions
 
## ❑ Fetching instructions involves


- ❑ reading the instruction from the Instruction Memory
- ❑ updating the PC value to be the address of the next (sequential) instruction



- ❑ PC is updated every clock cycle, so it does not need an explicit write control signal just a clock signal
- ❑ Reading from the Instruction Memory is a combinational activity, so it doesn't need an explicit read control signal
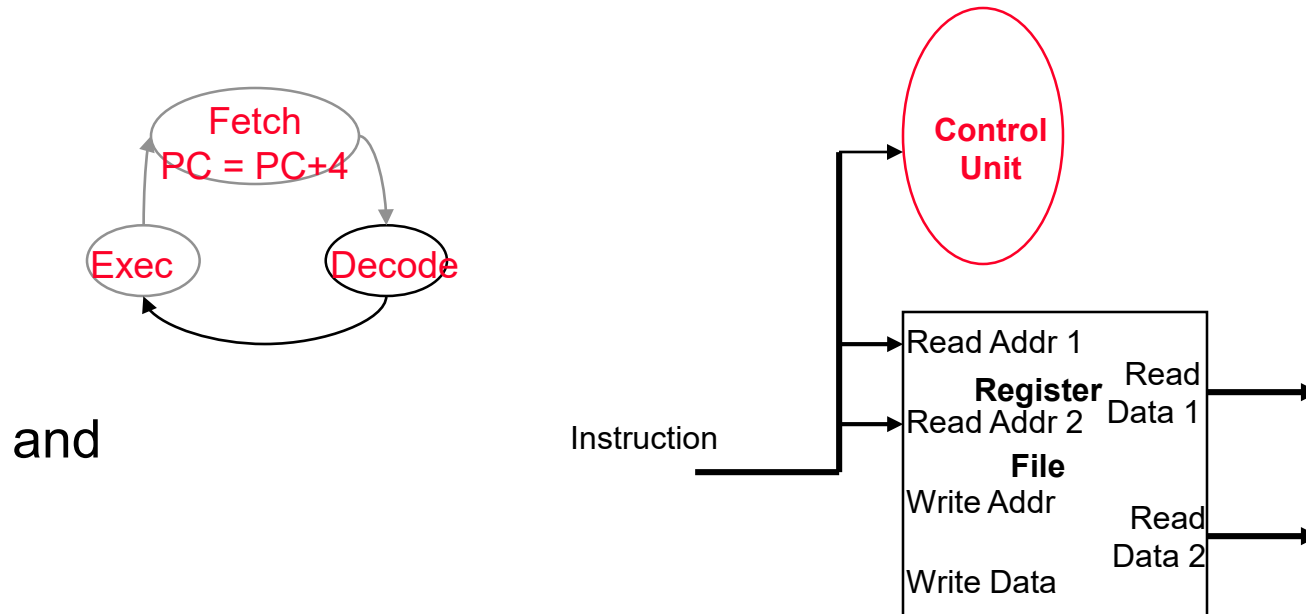
# Decoding Instructions


- ❑ Decoding instructions involves
  - ❑ sending the fetched instruction's opcode and function field bits to the control unit




- ❑ reading two values from the Register File
  - Register File addresses are contained in the instruction
 
# Executing R Format Operations

- R format operations (**add**, **sub**, **and**, **or**)



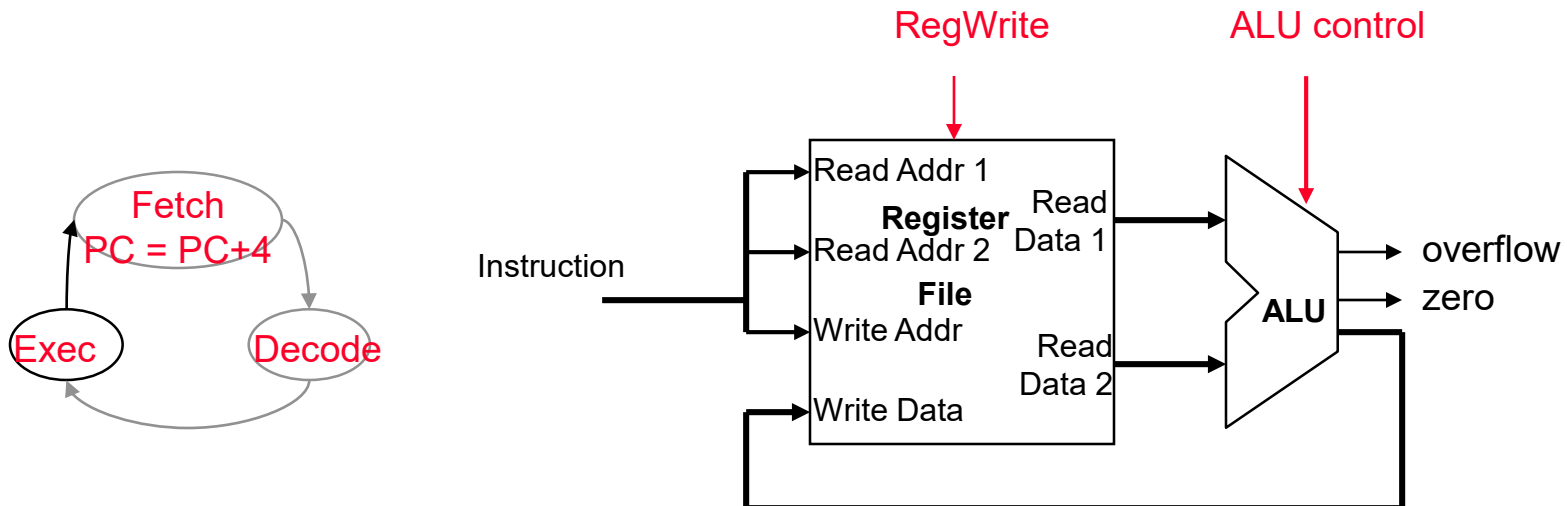
- perform operation (**op** and **funct**) on values in **rs1** and **rs2**
- store the result back into the Register File (into location **rd**)



- Note that Register File is not written every cycle (e.g. **sd**), so we need an explicit write control signal for the Register File
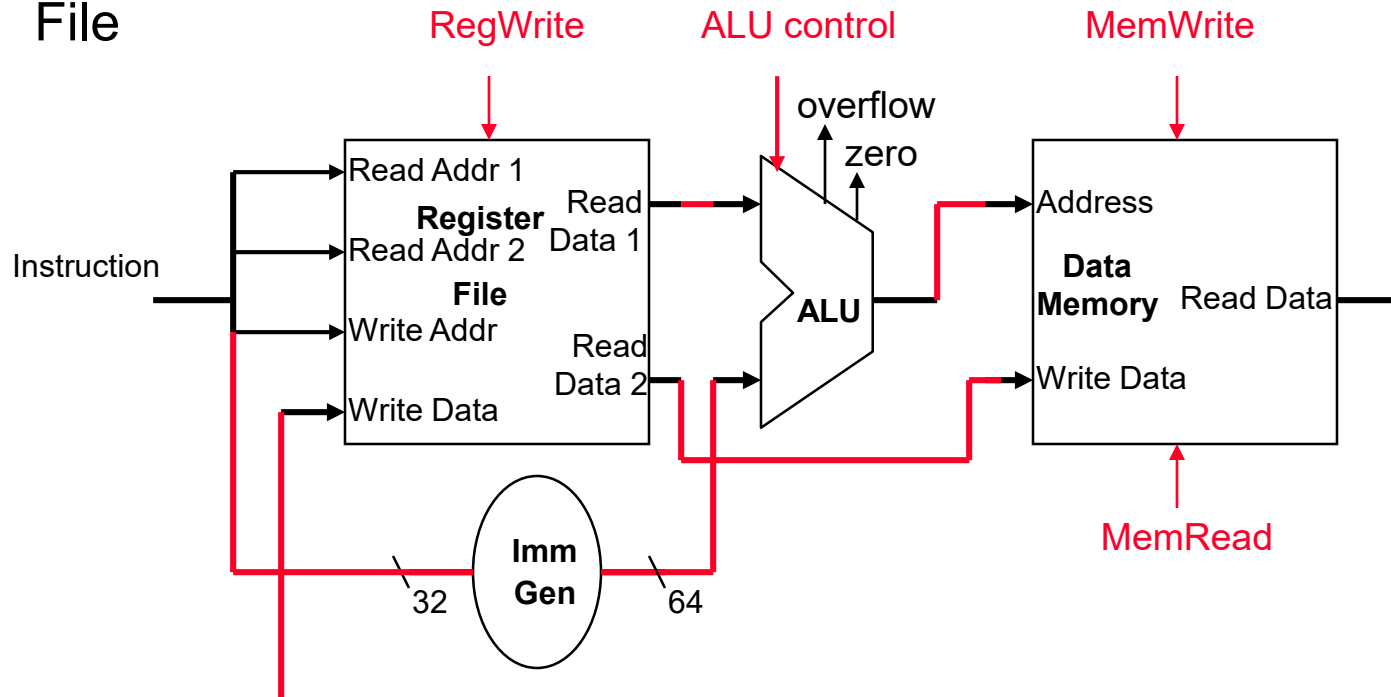
# Executing Load and Store Operations


- ❑ Load and store operations involves
  - ❑ compute memory address by adding the base register (read from the Register File during decode) to the 12-bit signed-extended offset field in the instruction
  - ❑ **store** value (read from the Register File during decode) written to the Data Memory
  - ❑ **load** value, read from the Data Memory, written to the Register File



# Executing Branch Operations
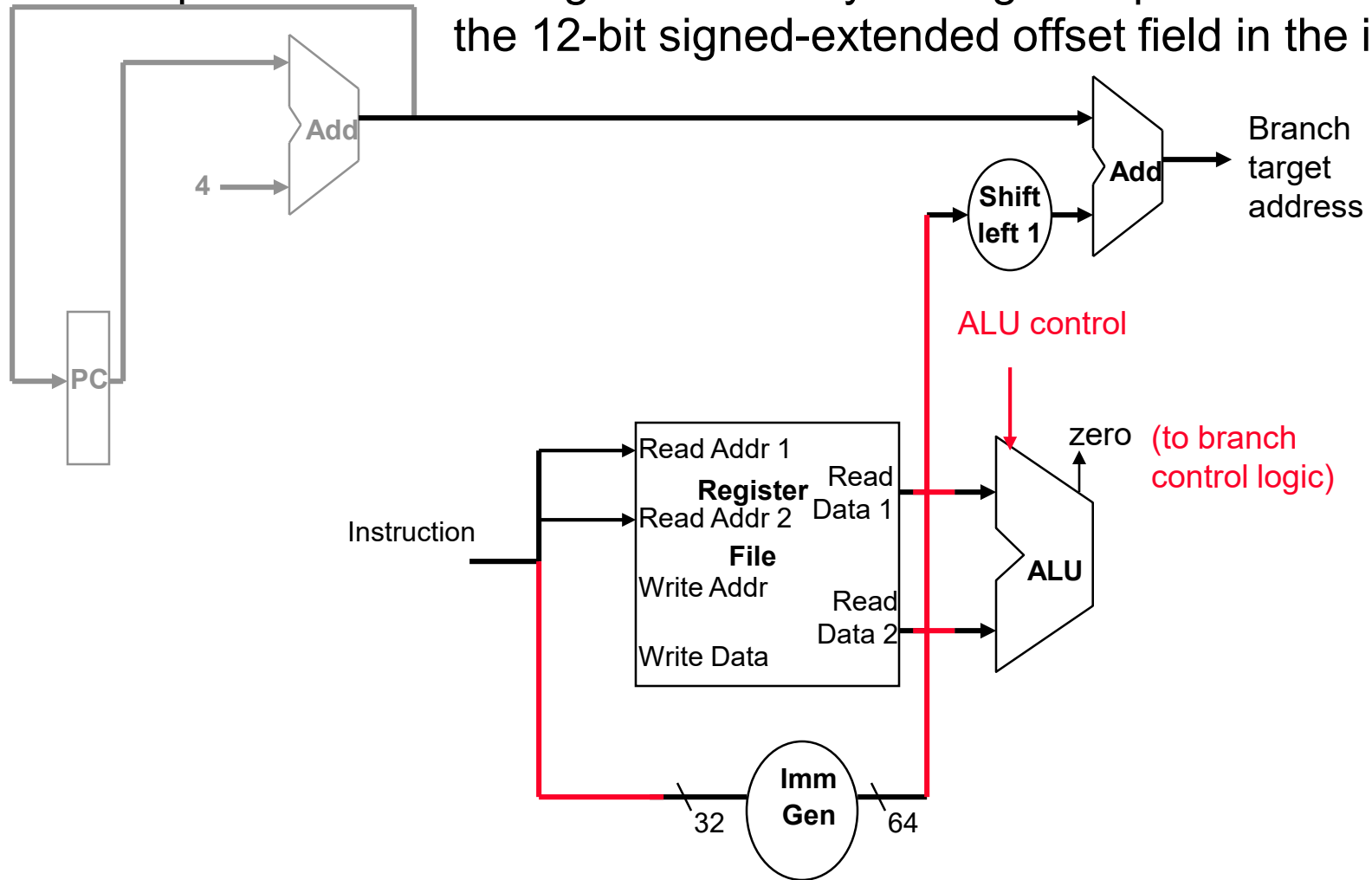
## ❑ Branch operations involves

- ❑ compare the operands read from the Register File during decode for equality (**zero** ALU output)
- ❑ compute the branch target address by adding the updated PC to the 12-bit signed-extended offset field in the instr






# Creating a Single Datapath from the Parts


- ❑ Assemble the datapath segments and add control lines and multiplexors as needed
- ❑ **Single cycle** design – fetch, decode and execute each instructions in **one** clock cycle
  - ❑ no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)
  - ❑ **multiplexors** needed at the input of shared elements with control lines to do the selection
  - ❑ write signals to control writing to the Register File and Data Memory
- ❑ Cycle time is determined by length of the longest path

# Fetch, R, and Memory Access Portions

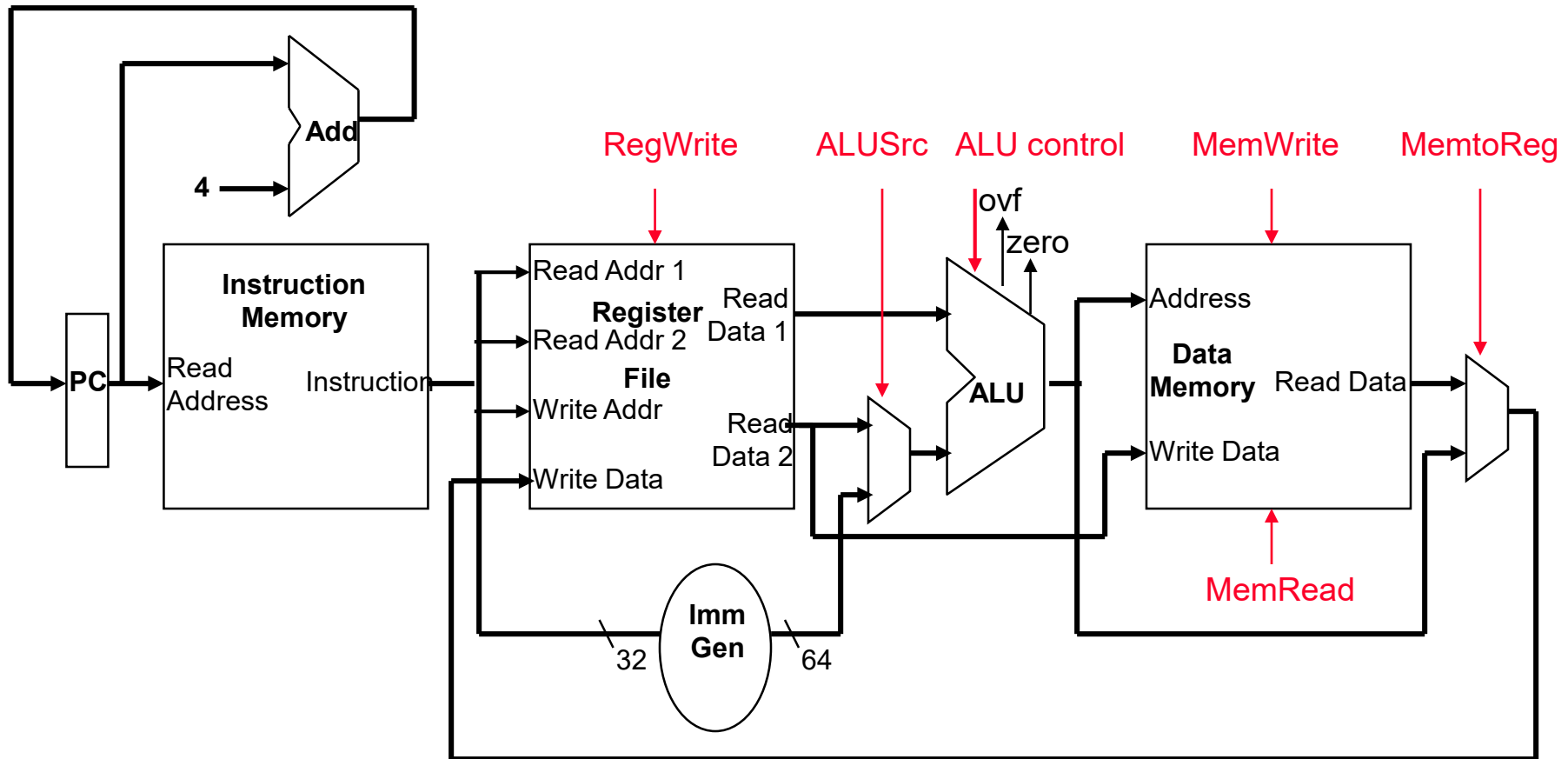
 
# Adding the Control


- ❑ Selecting the operations to perform (ALU, Register File and Memory read/write)
- ❑ Controlling the flow of data (multiplexor inputs)




## ❑ Observations

- ❑ op field always in bits 0-6
- ❑ addr of registers to be read are always specified by the rs1 field (bits 15-19) and rs2 field (bits 20-24); for ld and sd rs1 is the base register
- ❑ addr. of register to be written is always in rd (bits 7-11) for ld and R-type instructions

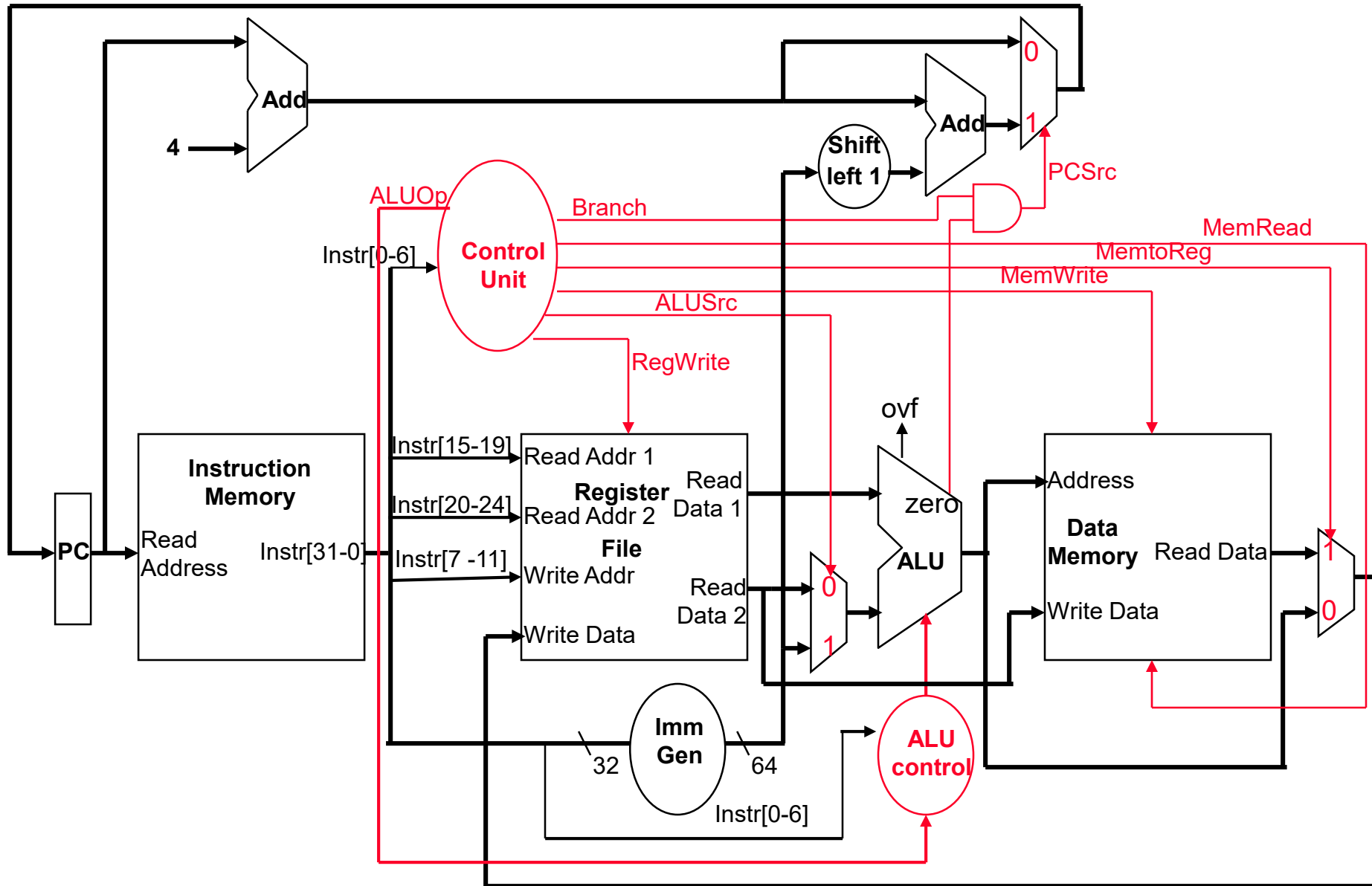
# Single Cycle Datapath with Control Unit




# R-type Instruction Data/Control Flow

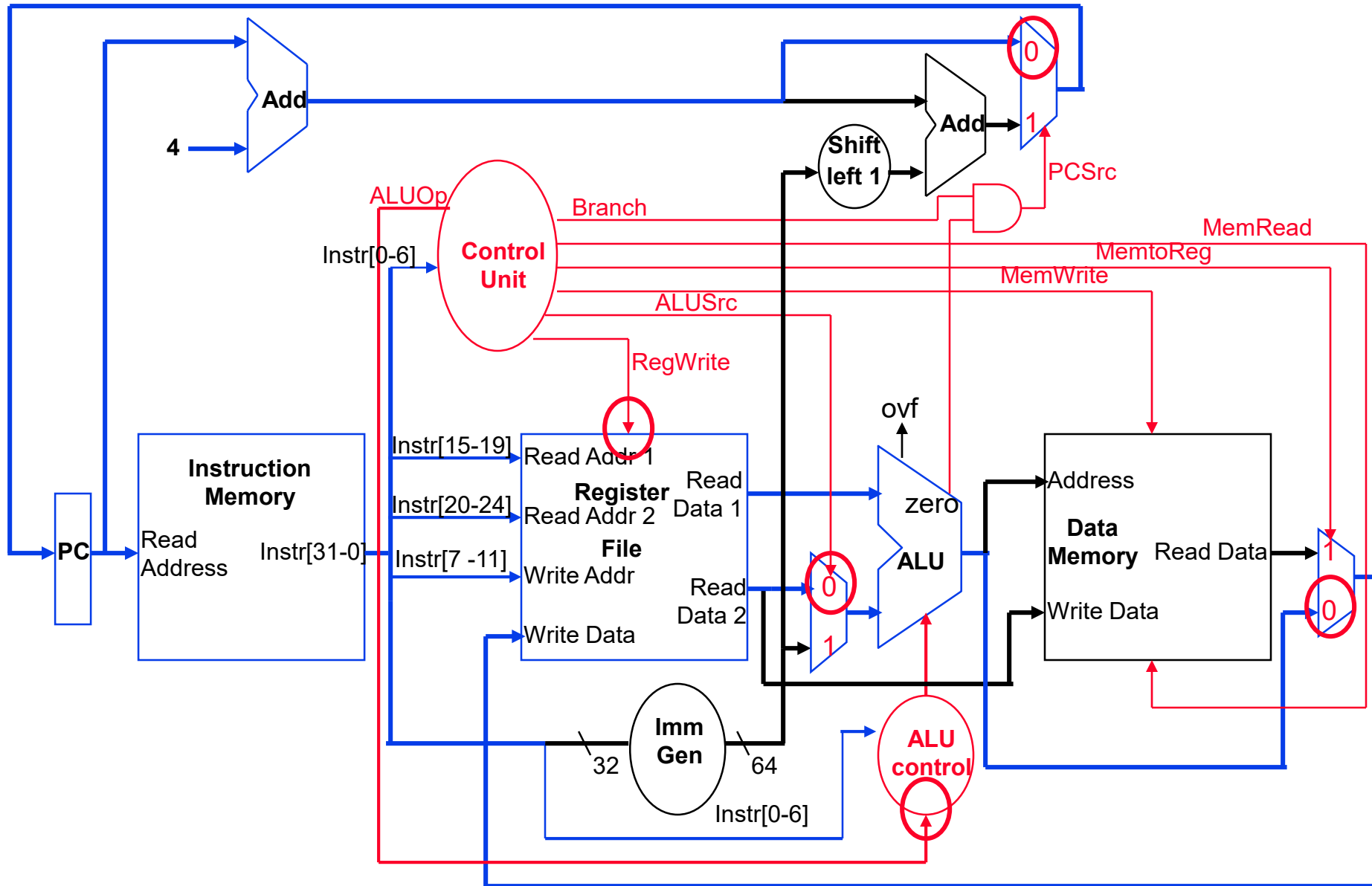
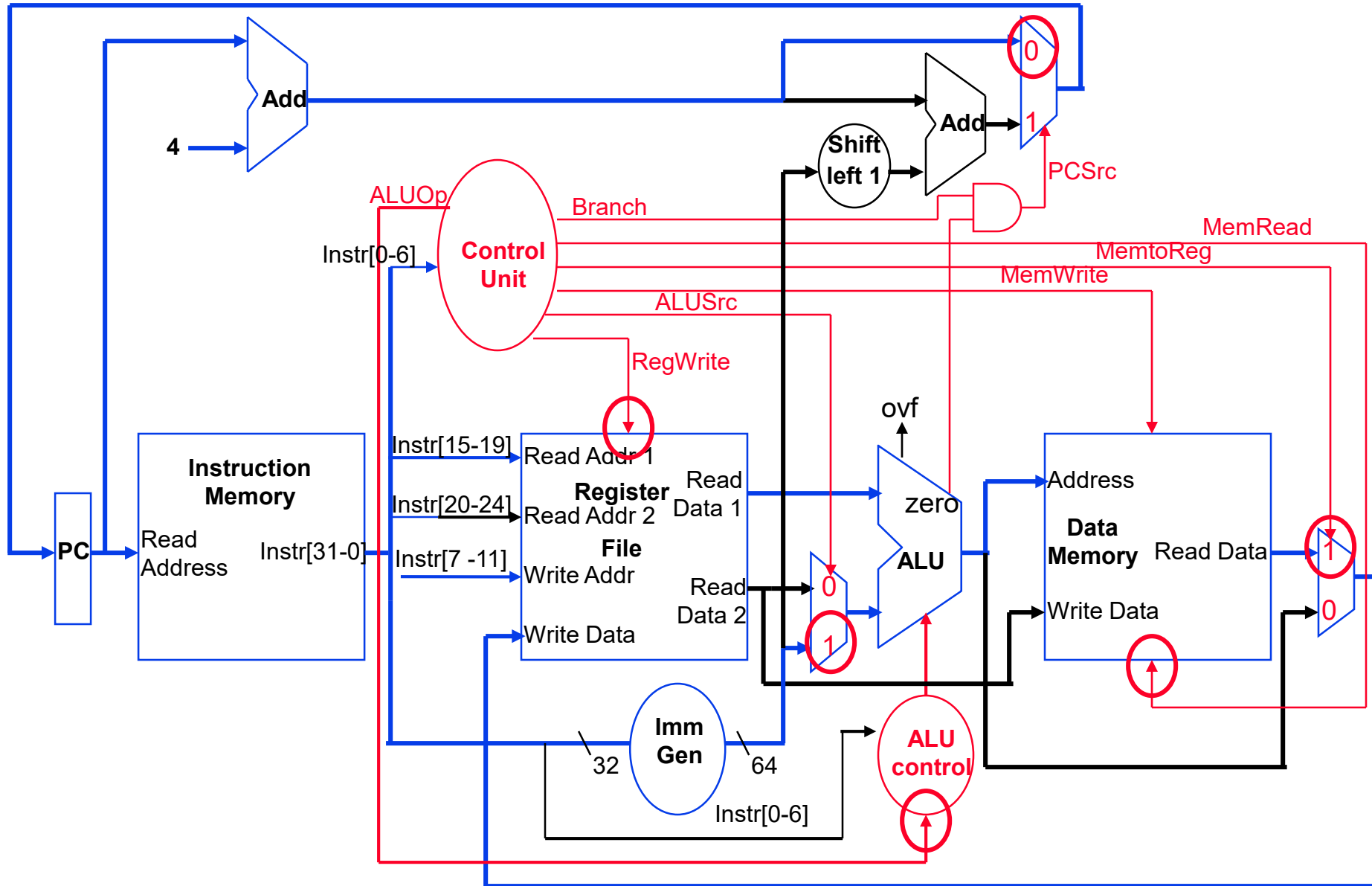
# Load Word Instruction Data/Control Flow



# Branch Instruction Data/Control Flow

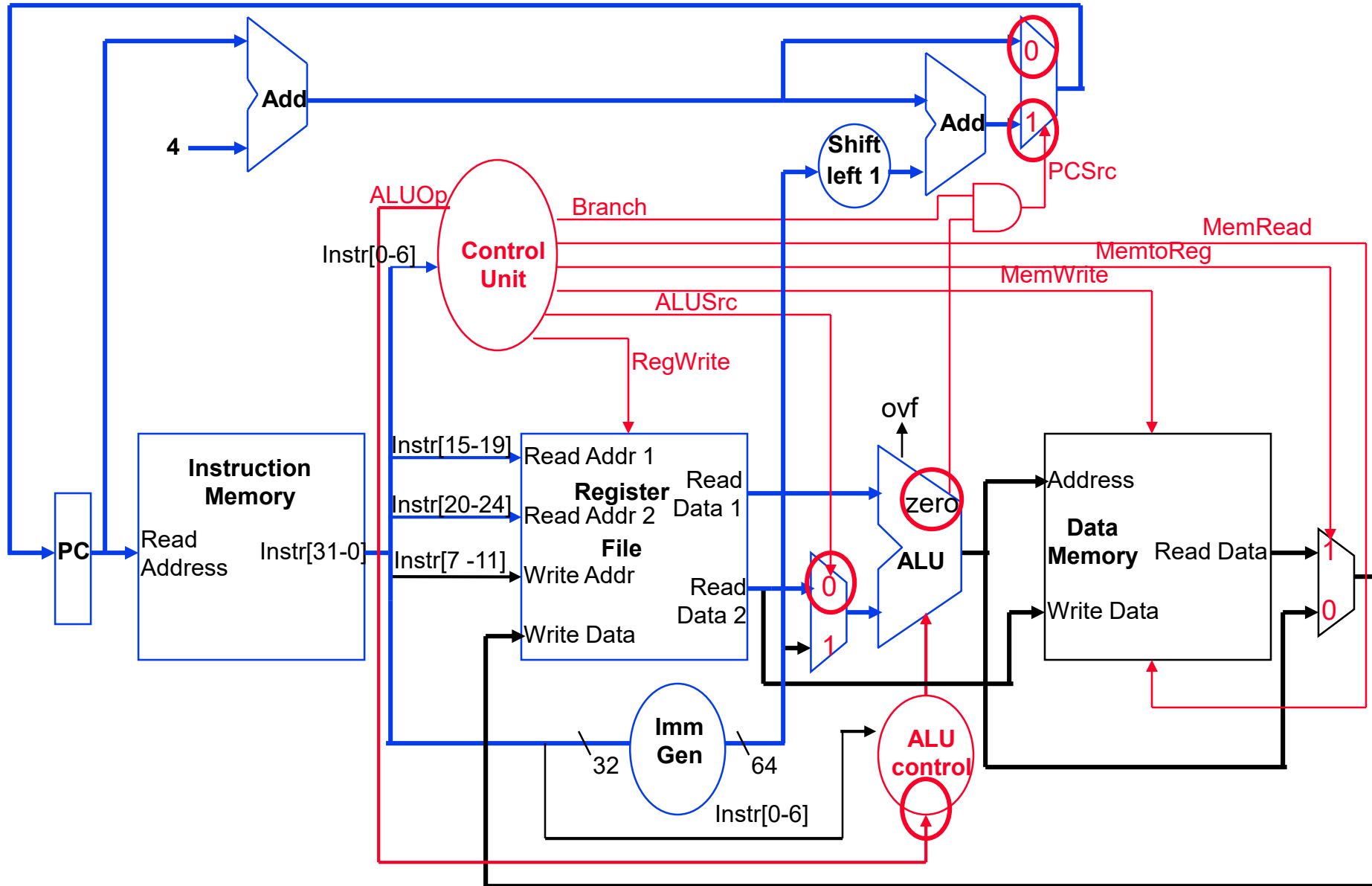

# Instruction Critical Paths

❑ What is the clock cycle time assuming negligible delays for muxes, control unit, sign extend, PC access, shift left 2, wires, setup and hold times except:


- ❑ Instruction and Data Memory (200 ps)
- ❑ ALU and adders (200 ps)
- ❑ Register File access (reads or writes) (100 ps)

Instr.	I Mem	Reg Rd	ALU Op	D Mem	Reg Wr	Total
R-type	200	100	200		100	600
load	200	100	200	200	100	800
store	200	100	200	200		700
beq	200	100	200			500


 
# Single Cycle Disadvantages & Advantages

- ❑ Uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the **slowest** instruction
  - ❑ especially problematic for more complex instructions like floating point multiply



- ❑ May be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle


but

- ❑ Is simple and easy to understand

# How Can We Make It Faster?

- ❑ Start fetching and executing the next instruction before the current one has completed
  - ❑ **Pipelining** – (all?) modern processors are pipelined for performance
  - ❑ Remember *the* performance equation:
$$\text{CPU time} = \text{CPI} * \text{TC} * \text{IC}$$
- ❑ Under *ideal* conditions and with a large number of instructions, the speedup from pipelining is approximately equal to the number of pipe stages
  - ❑ A five stage pipeline is nearly five times faster because the TC is nearly five times faster
- ❑ Fetch (and execute) more than one instruction at a time
  - ❑ Superscalar processing – stay tuned


# The Five Stages of Load Instruction

 

- ❑ IFetch: Instruction Fetch and Update PC
- ❑ Dec: Registers Fetch and Instruction Decode
- ❑ Exec: Execute R-type; calculate memory address
- ❑ Mem: Read/write the data from/to the Data Memory
- ❑ WB: Write the result data into the register file
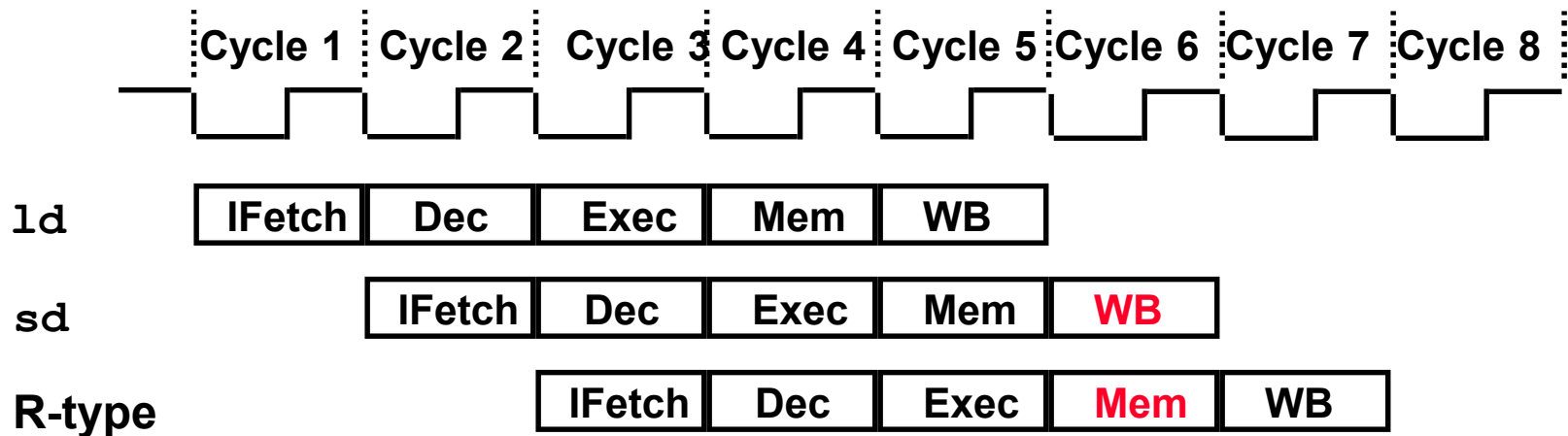
# A Pipelined RISC-V Processor


- ❑ Start the **next** instruction before the current one has completed
  - ❑ improves **throughput** - total amount of work done in a given time
  - ❑ instruction **latency** (execution time, delay time, response time - time from the start of an instruction to its completion) is *not* reduced




- clock cycle (pipeline stage time) is limited by the **slowest** stage
  - for some stages don't need the whole clock cycle (e.g., WB)
  - for some instructions, some stages are **wasted** cycles (i.e., nothing is done during that cycle for that instruction)

# Single Cycle versus Pipeline

 **Single Cycle Implementation (TC = 800 ps):**



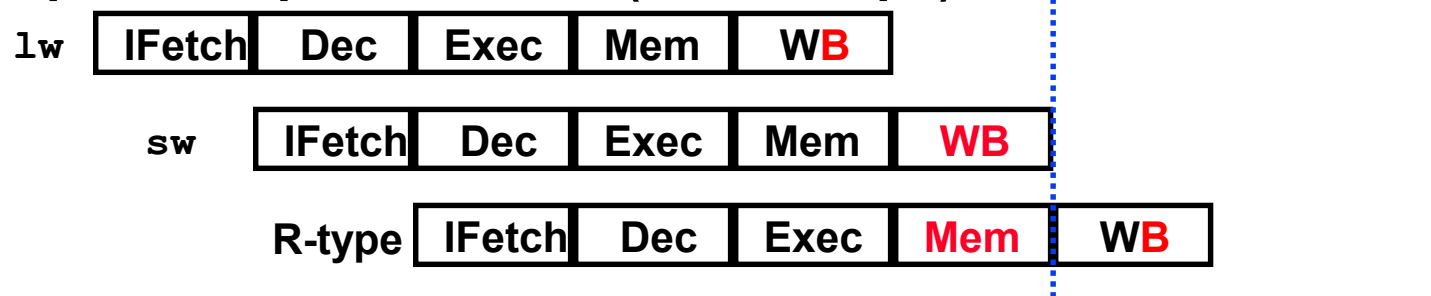**Pipeline Implementation (TC = 200 ps):**



- ❑ To complete an entire instruction in the pipelined case takes 1000 ps (as compared to 800 ps for the single cycle case). Why ?
- ❑ How long does each take to complete 1,000,000 adds ?


# Pipelining the RISC-V ISA

## ❑ What makes it easy

- ❑ all instructions are the same length (32 bits)
  - can fetch in the 1<sup>st</sup> stage and decode in the 2<sup>nd</sup> stage
- ❑ few instruction formats (three)
  - can begin reading register file in 2<sup>nd</sup> stage
- ❑ memory operations occur only in loads and stores
  - can use the execute stage to calculate memory addresses
- ❑ each instruction writes at most one result (i.e., changes the machine state) and does it in the last few pipeline stages (MEM or WB)

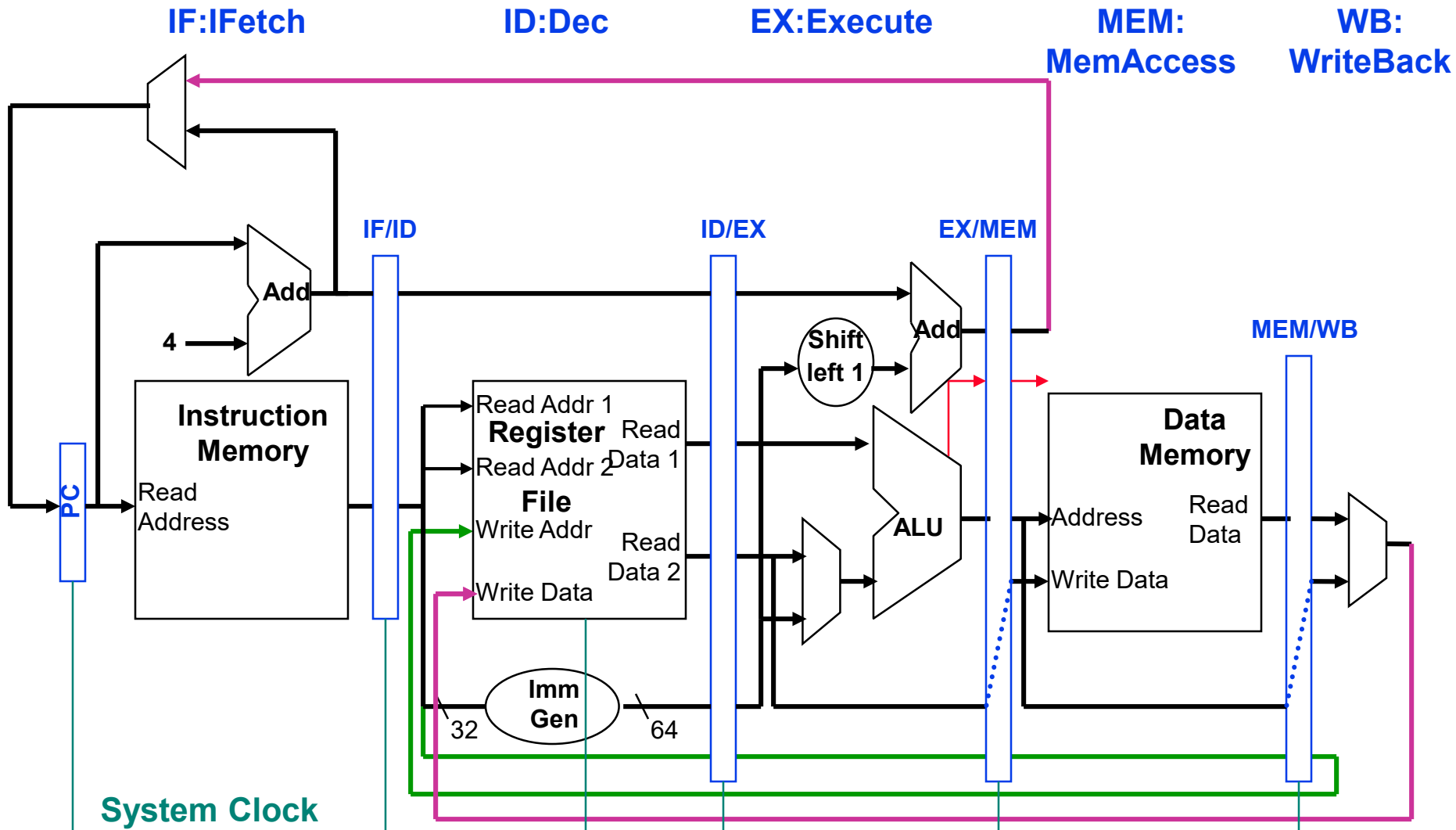
# RISC-V Pipeline Datapath Additions/Mods

- ❑ State registers between each pipeline stage to **isolate** them


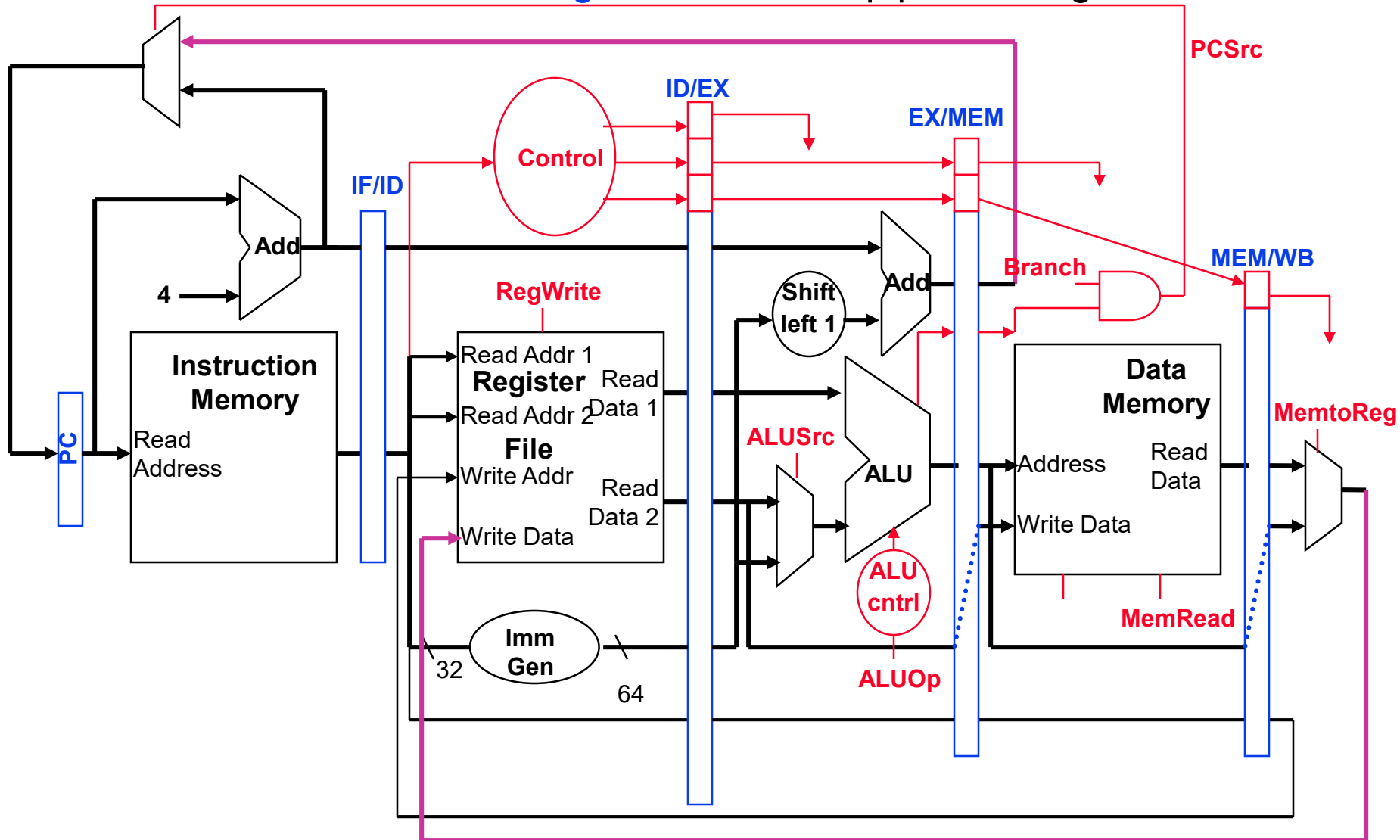
# RISC-V Pipeline Control Path Modifications

- ❑ All control signals can be determined during Decode
- ❑ and held in the **state registers** between pipeline stages






# Pipeline Control

- ❑ IF Stage: read Instr Memory (always asserted) and write PC (on System Clock)
- ❑ ID Stage: no optional control signals to set

	EX Stage				MEM Stage			WB Stage	
	Reg Dst	ALU Op1	ALU Op0	ALU Src	Brch	Mem Read	Mem Write	Reg Write	Mem toReg
R	1	1	0	0	0	0	0	1	0
ld	0	0	0	1	0	1	0	1	1
sd	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X

 
# Graphically Representing RISC-V Pipeline



- ❑ Can help with answering questions like:
  - ❑ How many cycles does it take to execute this code?
  - ❑ What is the ALU doing during cycle 4?
  - ❑ Is there a hazard, why does it occur, and how can it be fixed?

# Why Pipeline? For Performance!

Time (clock cycles)

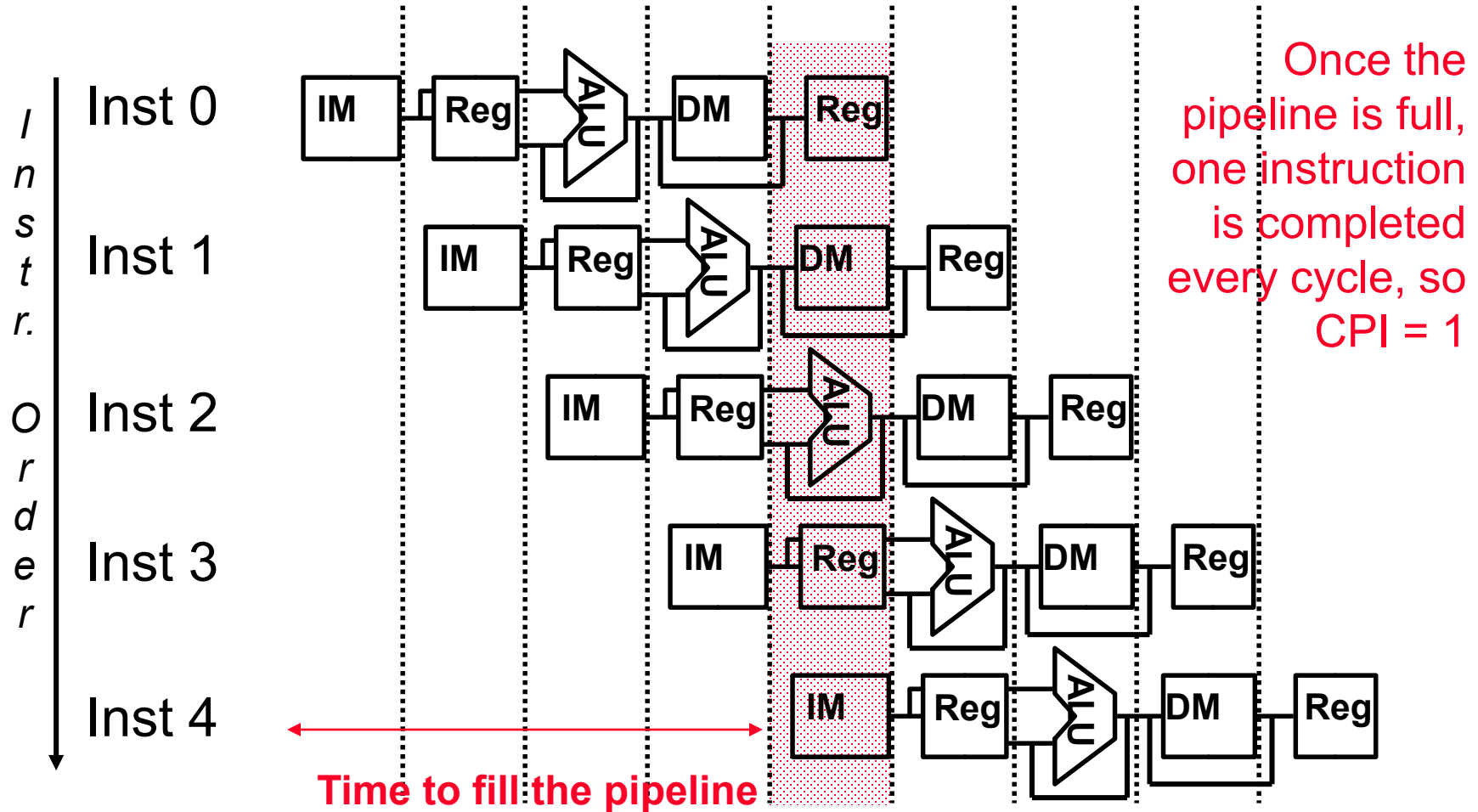

# Can Pipelining Get Us Into Trouble?


## ❑ Yes: Pipeline Hazards

- ❑ **structural hazards**: attempt to use the same resource by two different instructions at the same time
- ❑ **data hazards**: attempt to use data before it is ready
  - An instruction's source operand(s) are produced by a prior instruction still in the pipeline
- ❑ **control hazards**: attempt to make a decision about program control flow before the condition has been evaluated and the new PC target address calculated
  - branch and jump instructions, exceptions

## ❑ Can usually resolve hazards by waiting

- ❑ pipeline control must **detect** the hazard
- ❑ and take action to **resolve** hazards

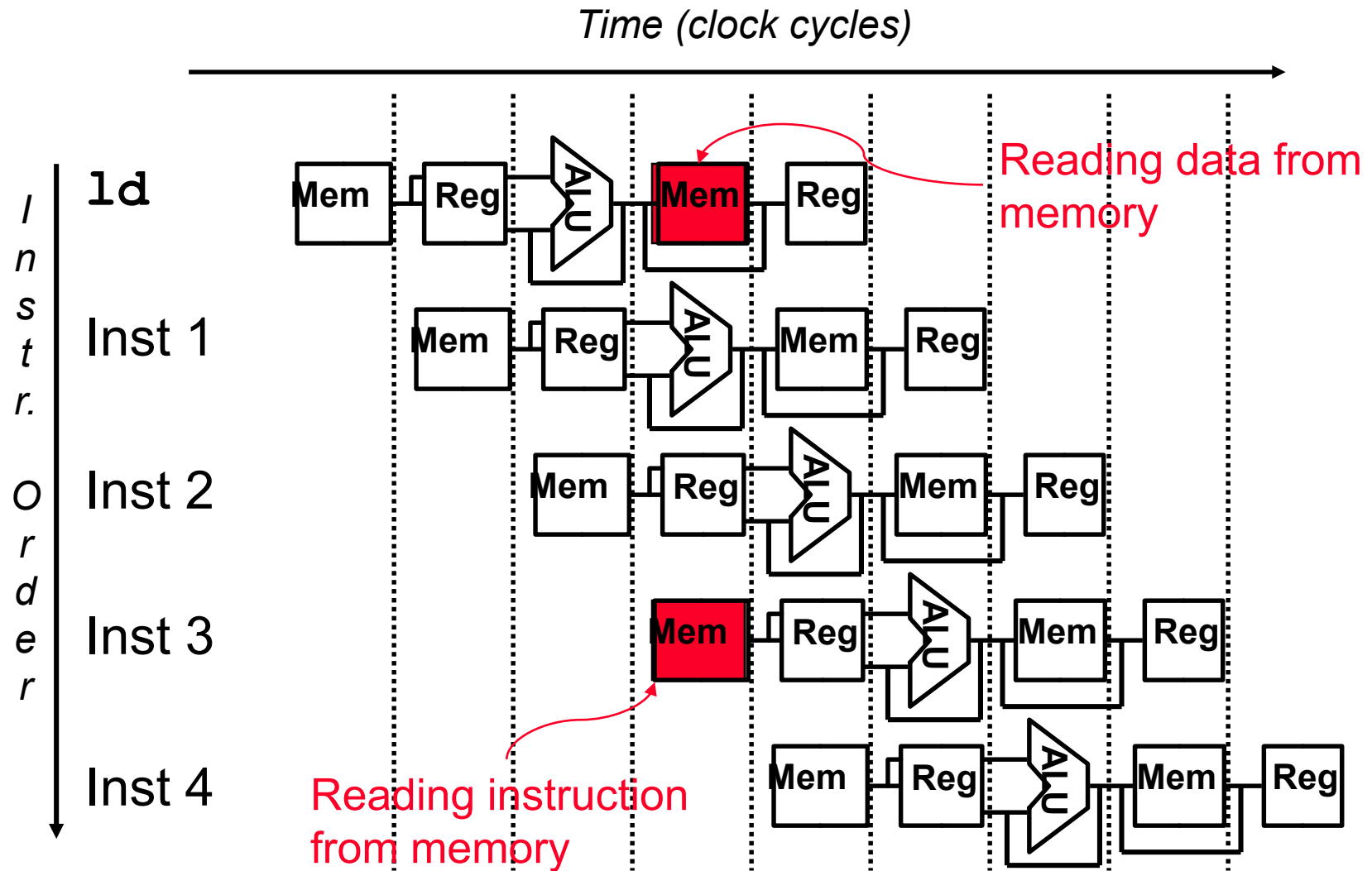
# A Single Memory Would Be a Structural Hazard



□ Fix with separate instr and data memories (I\$ and D\$)


# How About Register File Access?

Time (clock cycles)

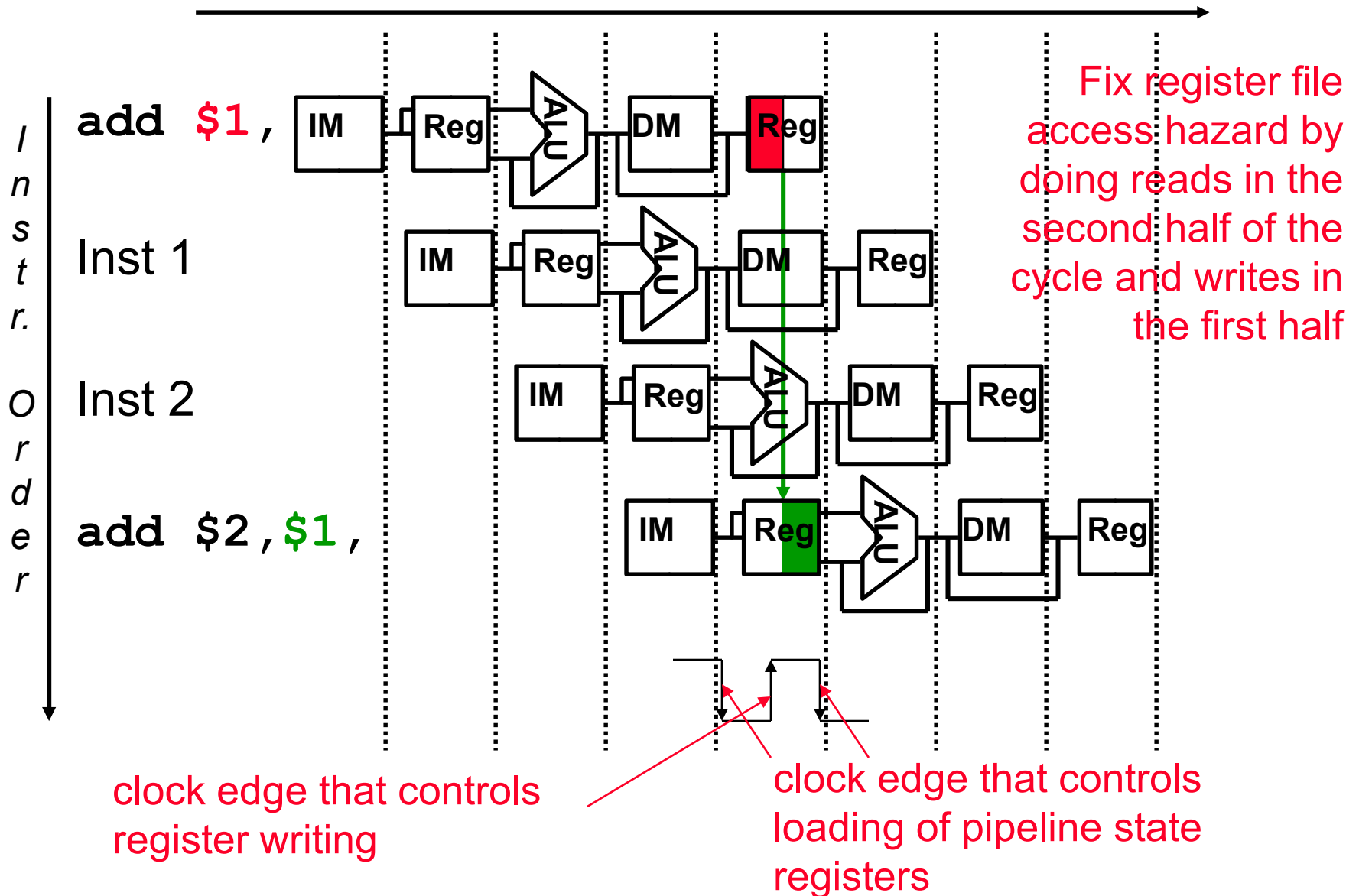
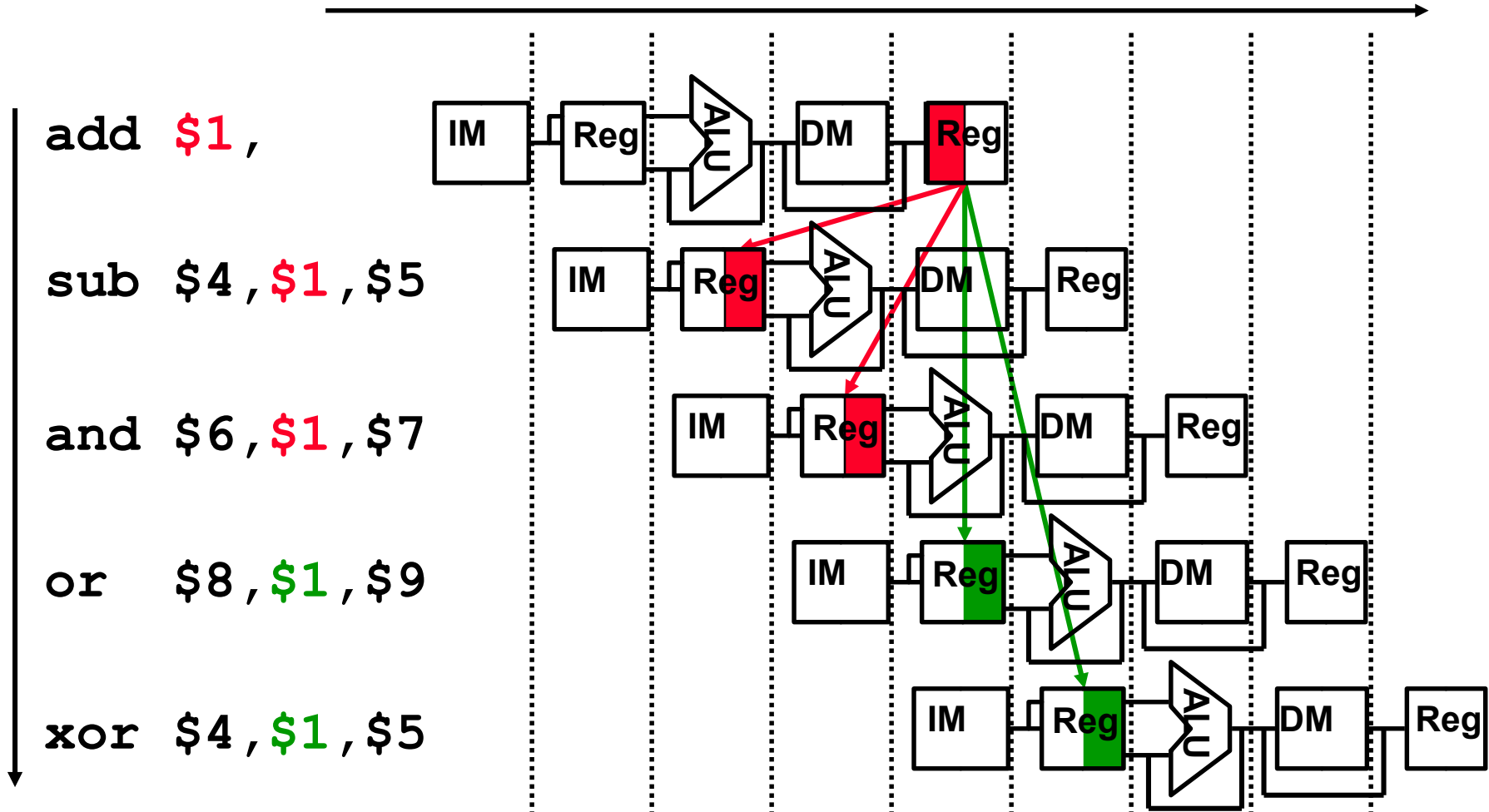
# Register Usage Can Cause Data Hazards


❑ Dependencies backward in time cause **hazards**



❑ Read before write **data hazard**
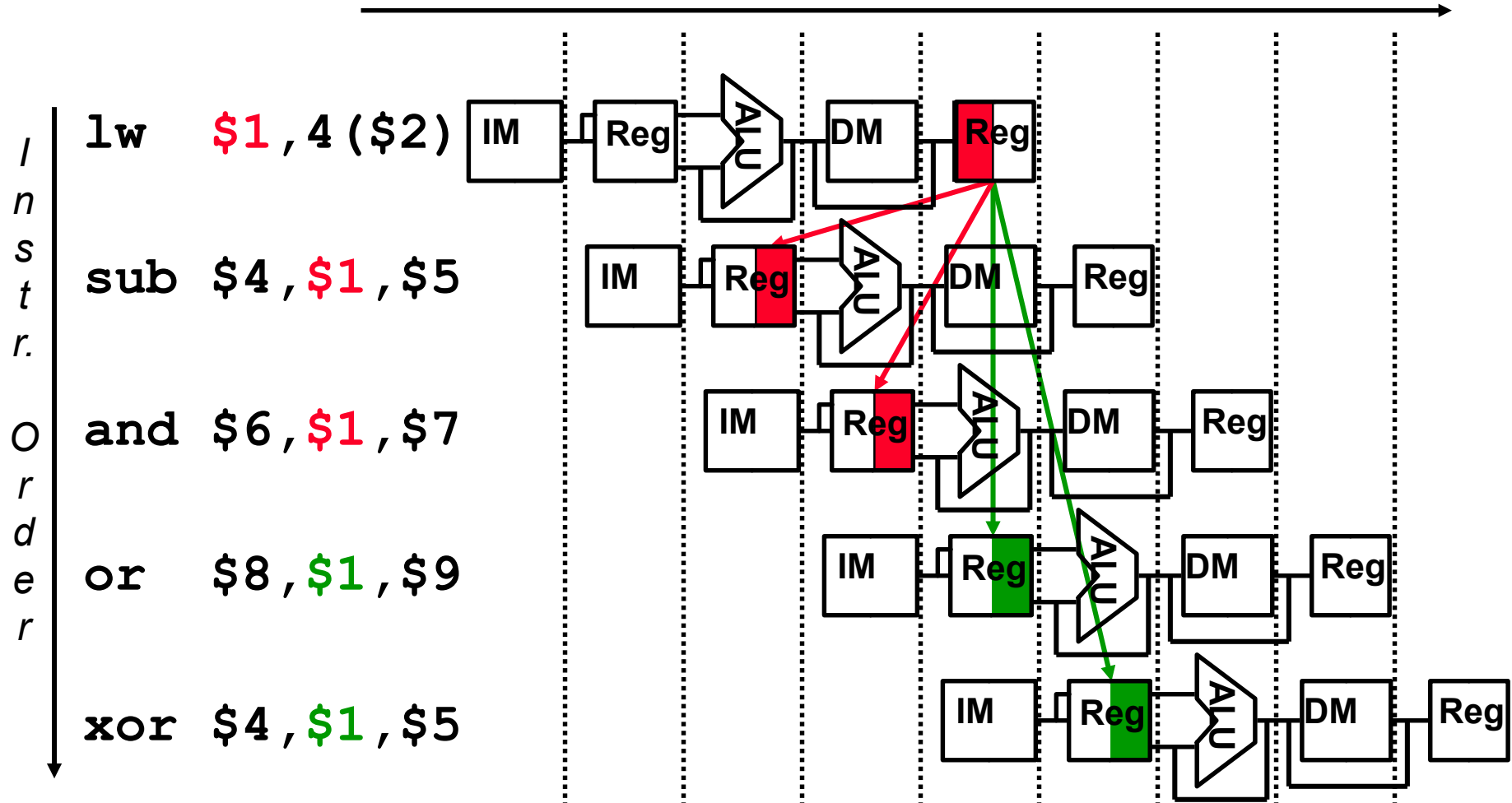
# Loads Can Cause Data Hazards

❑ Dependencies backward in time cause **hazards**




❑ Load-use data hazard



 
# Branch Instructions Cause Control Hazards

- Dependencies backward in time cause **hazards**



 
# Other Pipeline Structures Are Possible

- ❑ What about the (slow) multiply operation?
  - ❑ Make the clock twice as slow or ...
  - ❑ let it take two cycles (since it doesn't use the DM stage)




 - ❑ What if the data memory access is twice as slow as the instruction memory?
  - ❑ make the clock twice as slow or ...
  - ❑ let data memory access take two cycles (and keep the same clock rate)




# Other Sample Pipeline Alternatives

## ARM7

 

## XScale

 

# Summary

- ❑ All modern day processors use pipelining
- ❑ Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- ❑ Potential speedup: a CPI of 1 and fast TC
- ❑ Pipeline rate limited by **slowest** pipeline stage
  - ❑ Unbalanced pipe stages makes for inefficiencies
  - ❑ The time to “**fill**” pipeline and time to “**drain**” it can impact speedup for deep pipelines and short code runs
- ❑ Must detect and resolve hazards
  - ❑ Stalling negatively affects CPI (makes CPI less than the ideal of 1)